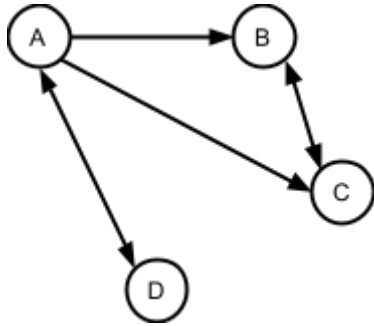


# American Computer Science League

2021-2022 • Contest 4: Short Problems • Senior Division

## 1. Graph Theory


What is the shortest path length that will have more than one path between two vertices in the following directed graph?



- A. 1
- B. 2
- C. 3
- D. 4
- E. 5
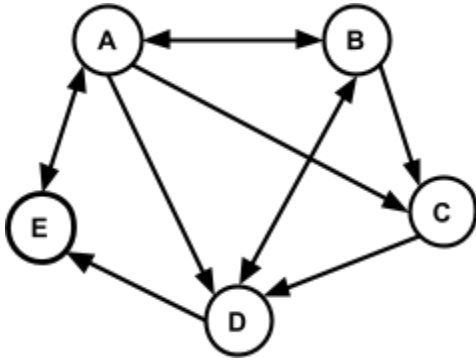
## 2. Graph Theory


How many cycles are there in the following directed graph?



- A. 5
- B. 7
- C. 9
- D. 10
- E. 12
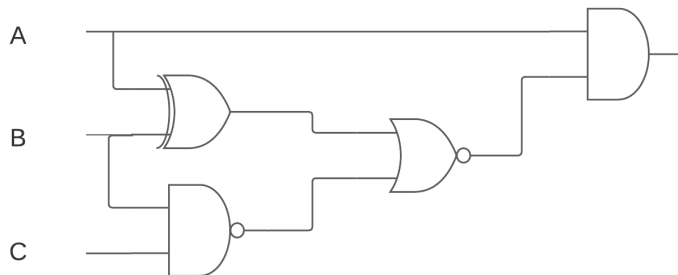
## 3. Digital Electronics


Simplify the Boolean expression of this digital circuit.



- A.  $A B C$
- B.  $\overline{A} B C$
- C.  $A \overline{B} C$
- D.  $A B \overline{C}$
- E.  $\overline{A B C}$
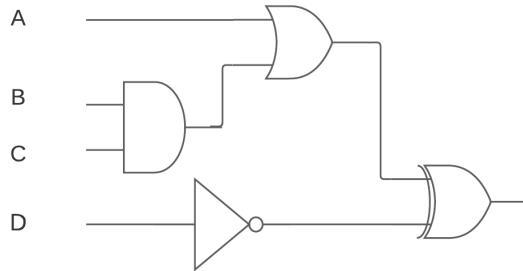
#### 4. Digital Electronics

How many ordered quadruples make the following digital circuit TRUE?



- A. 0
- B. 4
- C. 8
- D. 12
- E. 16

#### 5. Assembly Language

What is printed when the following program is executed?

```
N      DC      5
      LOAD     N
      STORE    F
      SUB      =1
TOP    STORE    B
      LOAD     F
      MULT     B
      STORE    F
      LOAD     B
      SUB      =1
      BE       OUT
      LOAD     B
      SUB      =1
      BU       TOP
OUT    PRINT    F
      END
```

- A. 15
- B. 30
- C. 60
- D. 120
- E. 240